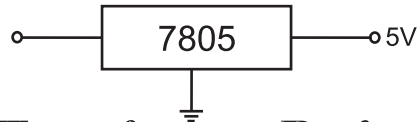


Power Supply Component Design




Transformer Design

We require +5V o/p.

The drop-out voltage of regulator is 2V (As per datasheet).

$$V_{dc} = 5 + 2 = 7V$$

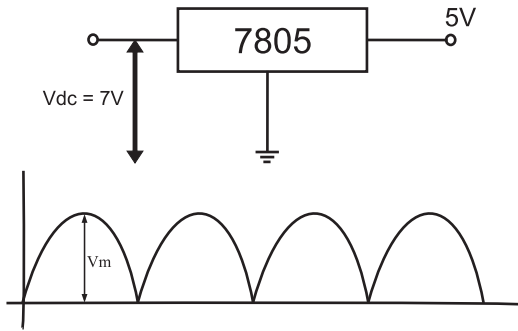So at the regulator input minimum 7V should be applied.



According to formula,

$$V_{dc} = 2V_m / \pi$$

Assuming there is no Ripple Capacitor
From

$$\begin{aligned} V_m &= V_{dc} \cdot \pi / 2 \\ &= 7 \times 3.14 / 2 \\ &= 10.99V \end{aligned}$$

$$V_m = 10.99V$$

During one cycle, two diode are conducting.

Drop of voltage of one diode = 0.7V

Drop of voltage of two diode = 1.4V

$$V_{im} = V_m + 1.4V$$

$$V_{im} = 10.99 + 1.4 = 12.39V$$

$$V_{im} = 12.39V$$

$$V_{rms} = V_{im} / \sqrt{2}$$

$$= 12.39 / \sqrt{2}$$

$$= 8.76V$$

$$V_{rms} = 8.76V$$

So we select transformer of 9V

Similarly $I_m = I_{dc} \times \pi / 2$

$$I_m = 400m \times 3.14 / 2$$

$$= 628mA$$

$$I_{rms} = I_m / \sqrt{2}$$

$$= 628m / \sqrt{2}$$

$$= 444.06mA$$

$$I_{rms} = 444.06mA$$

So we select transformer with current rating of 500mA.

Considering voltage and current transformer
we take **0-9V / 500mA**

**Transformer - 0-9V / 500mA Step
down transformer**


Rectifier Design

$$PIV \text{ of diode} = V_m = 12.39V$$

$$I_m = 628mA$$

So we select bridge IC of 1 Ampere rating.

Filter Capacitor Design

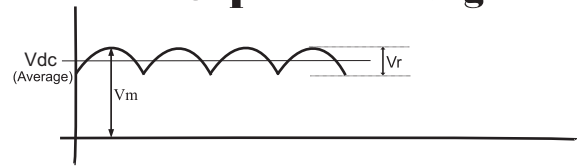


$$\begin{aligned} R &= V_{dc} / I_{dc} \\ &= 7 / 400m \\ &= 17.5 \Omega \end{aligned}$$

$$\begin{aligned} V_r &= 2(V_m - V_{dc}) \\ &= 2(12.39 - 7) \\ &= 10.78V \end{aligned}$$

$$\begin{aligned} C &= V_{dc} / (f \times R \times V_r) \\ &= 7 / (100 \times 17.5 \times 10.78) \\ &= 371.05\mu F \end{aligned}$$

So for safe working we select capacitor of 1000uF

$$C = 1000\mu F / 35V$$

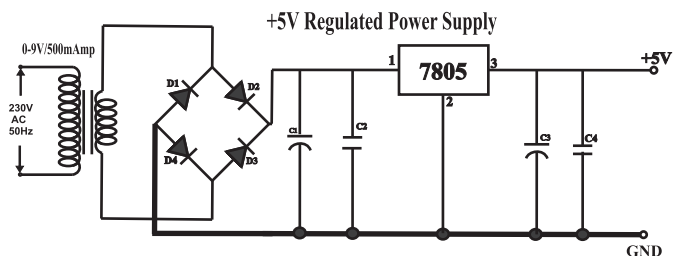

C1 - 1000uF/35V - Electrolytic Capacitor

C2,C4 - 0.1uF Ceramic Capacitor

C3 - 220uF/25V Electrolytic Capacitor